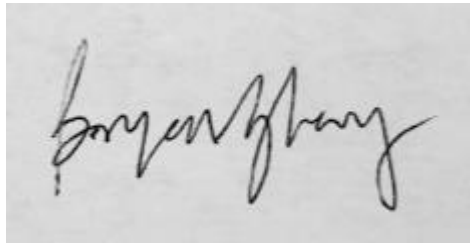


The University of British Columbia

# Mini Project 2

ELEC 301 – Electronic Circuits

A handwritten signature in black ink on a light gray background. The signature is written in a cursive style and appears to read "Bryan Zhang".

Bryan Zhang  
69238335  
10-24-2022

# Contents

|   |    |
|---|----|
| Part 1 .....  | 2  |
| a) 2N3904 datasheet lookup .....                      | 2  |
| b) 2N3904 characteristics .....                       | 2  |
| Comparing Measured value to datasheet values .....    | 5  |
| c) Biasing .....                                      | 5  |
| Biassing from measured plot (i) .....                 | 5  |
| Biassing using the 1/3 rule (ii) .....                | 6  |
| Using standard resistors (iii) .....                  | 7  |
| d) 2N2222A and 2N4401 d.c operating points (iv) ..... | 7  |
| Part 2 .....  | 8  |
| a) 2N3904 & 2N4401 Common Emitter Amplifier .....     | 8  |
| b) Midband Voltage Transfer Curve .....               | 11 |
| c) Input Impedance at midband .....                   | 12 |
| d) Output Impedance at midband .....                  | 12 |
| e) Transistor selection .....                         | 13 |
| Part 3 .....  | 13 |
| a) 2N2222A Common Base Amplifier poles & zeros .....  | 13 |
| b) Voltage Transfer Curve .....                       | 16 |
| c) Midband Input Impedance .....                      | 16 |
| d) Midband Output Impedance .....                     | 16 |
| References .....                                      | 17 |
| Appendix .....  | 18 |

## Part 1

### a) 2N3904 datasheet lookup

The datasheet values for the 2N3904 transistor at  $V_{CE} = 10V$ ,  $I_C = 1mA$ ,  $f = 1kHz$ , and  $T = 1kHz$  are shown below.

| Symbol             | Description       | Minimum        | Maximum       |
|--------------------|-------------------|----------------|---------------|
| $h_{fe} = \beta$   | DC Current Gain   | 100            | 400           |
| $h_{ie} = r_{\pi}$ | Input Impedance   | 1.0 k $\Omega$ | 10 k $\Omega$ |
| $h_{oe} = 1/r_o$   | Output Admittance | 1.0 $\mu$ mhos | 40 $\mu$ mhos |

### b) 2N3904 characteristics

Here is the circuit used to obtain the graph of  $I_b$  vs  $V_{BE}$ . I set  $V_{CE} = 5V$  and then sweep  $V_{BE}$  from 0 to 0.7V in 0.01V increments.

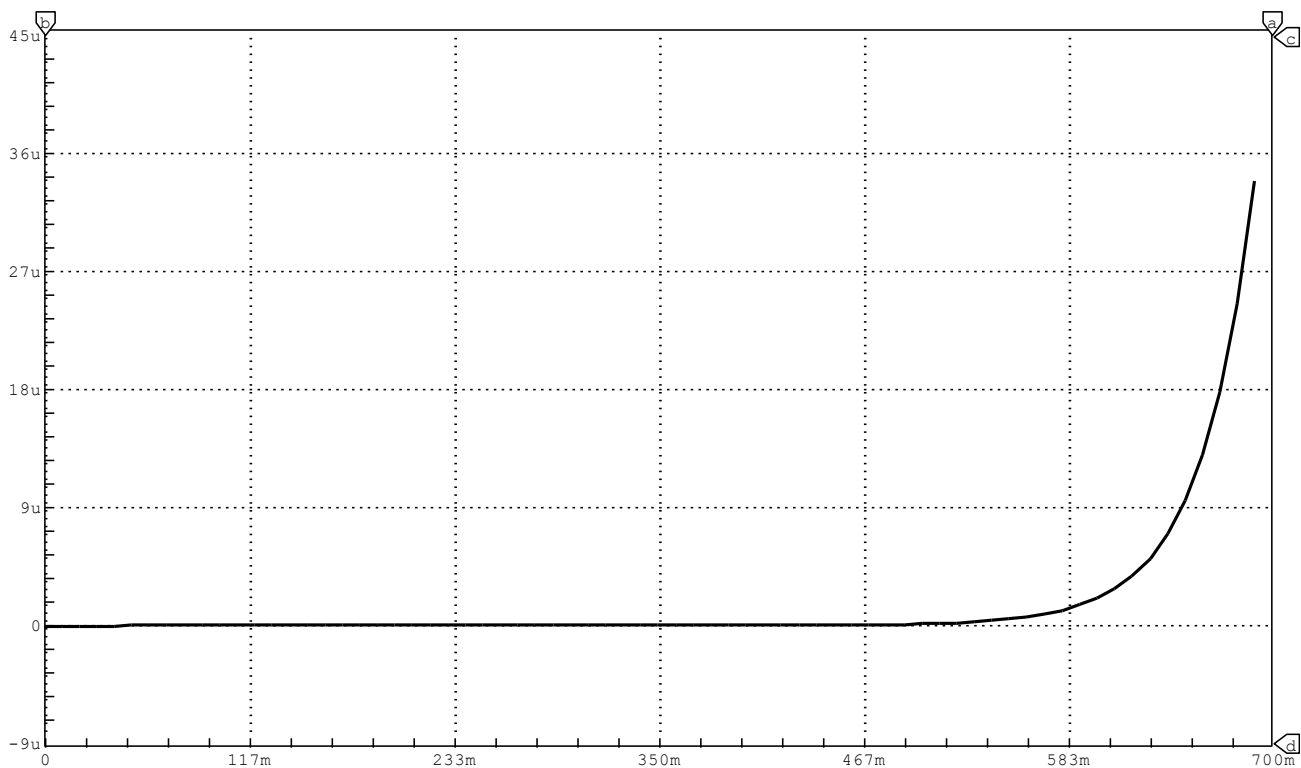
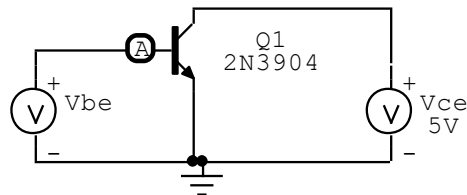


Figure 1:  $I_B$  vs  $V_{BE}$  graph

To find  $I_C$  vs  $V_{CE}$  with  $I_B$  as the varying parameter the circuit below is simulated.  $V_{CE}$  is swept from 0-6V in 20mV increments and  $I_B$  is swept from 1-10 $\mu$ A in 0.5 $\mu$ A increments.

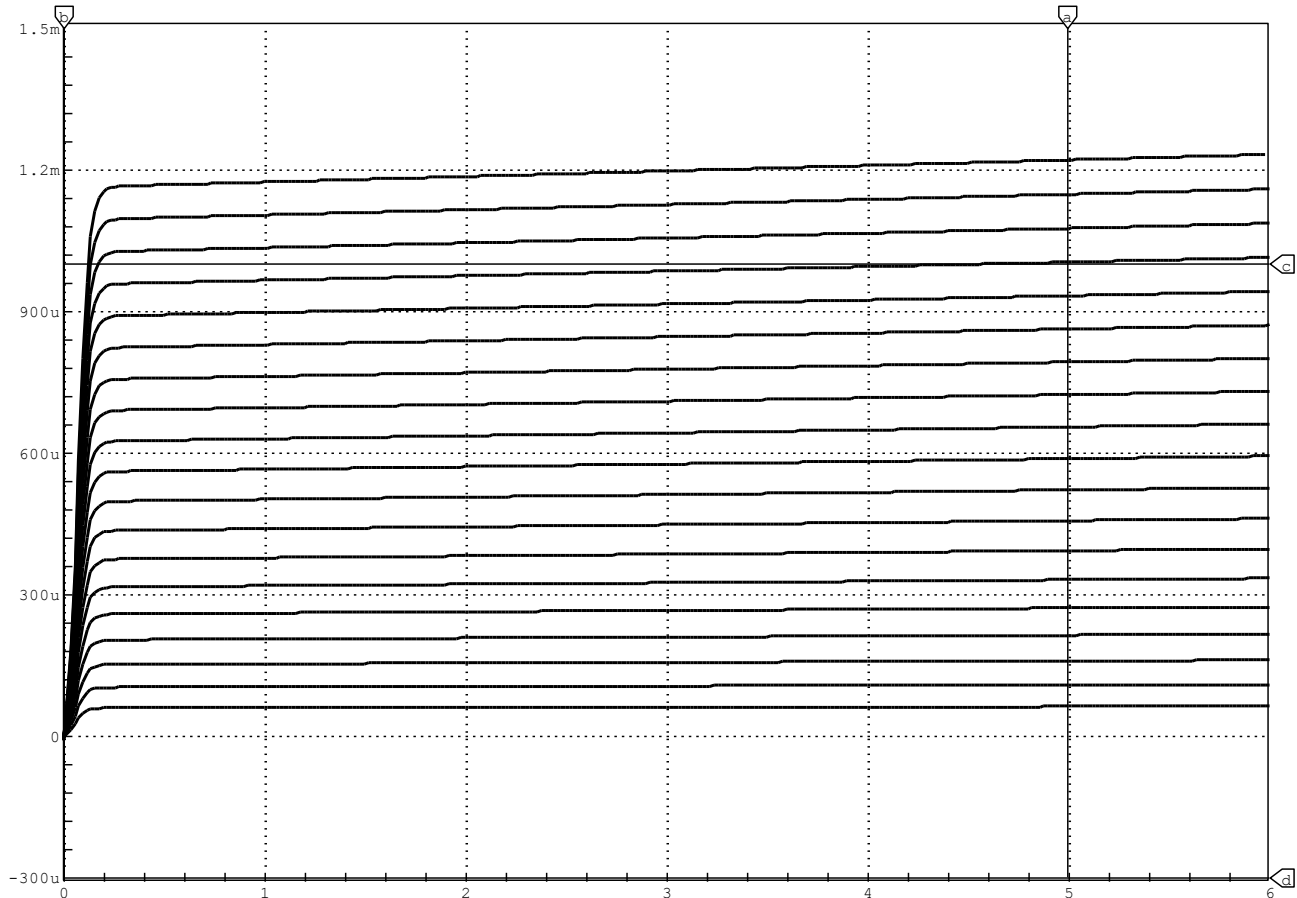
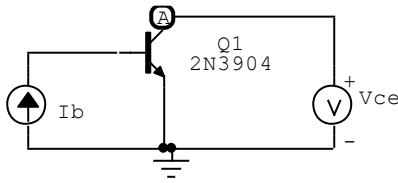


Figure 2:  $I_C$  vs  $V_{CE}$  with varying  $I_B$

Each line represents a different characteristic, with the bottom line being when  $I_B$  is 1  $\mu$ A and the top line when  $I_B$  is 10  $\mu$ A. The 'a' cursor is set to the value of  $V_{CE}=5$ V and the 'c' cursor is set to the value of  $I_C = 1$ mA. The intersection of the 2 cursors falls on the 3<sup>rd</sup> line from the top, so therefore


$$I_B = 10 - 3 \cdot 0.5 \mu A = \underline{8.5 \mu A}.$$

$$\longrightarrow \beta = \frac{I_C}{I_B} = \frac{1 \text{mA}}{8.5 \mu A} = \boxed{118}$$

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{mA}}{25 \text{mV}} = \boxed{0.04 \text{S}}$$

$$r_{\pi} = \frac{\beta}{g_m} = \boxed{2950\Omega}$$

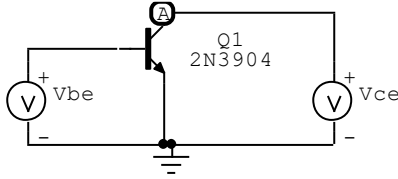Finally, we can find  $I_C$  vs  $V_{CE}$  with varying  $V_{BE}$  by simulating the below circuit.  $V_{CE}$  is the primary and is swept from 0-6V in 20mV increments, and  $V_{BE}$  is the secondary swept from 0.55-0.70V in 0.01V increments.



Xa: 5.000 Xb: 1.000 a-b: 4.000  
Yc: 6.607m Yd: 6.356m c-d: 251.9u

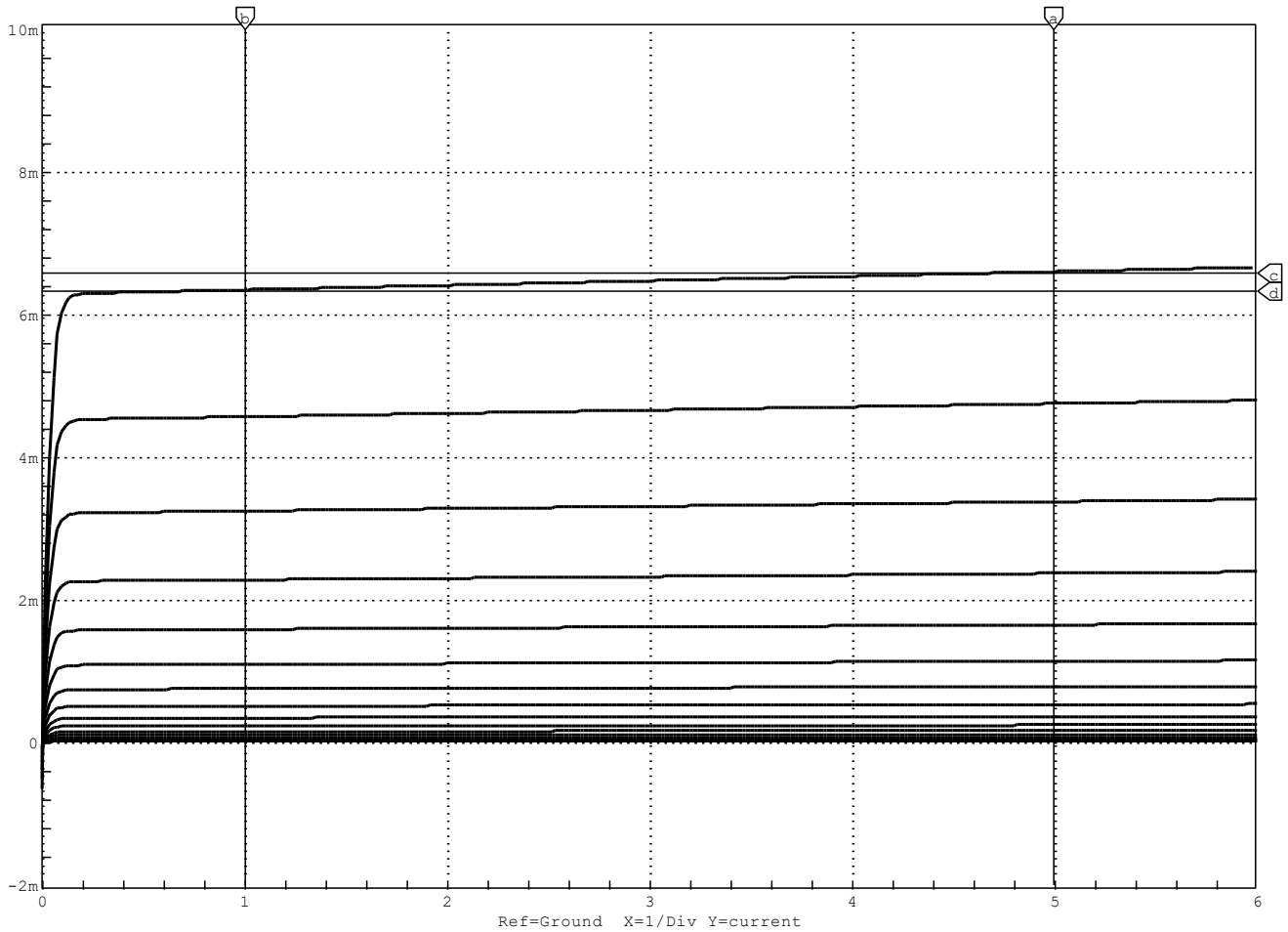


Figure 3:  $I_C$  vs  $V_{CE}$  with varying  $V_{BE}$

Observe that at  $I_C=1\text{mA}$  at the intersected curve corresponds to  $V_{BE} = 0.65\text{V}$ . The slope of the top curve can be calculated as  $m = \frac{c-d}{a-b}$  where a, b, c, d are the cursor positions.

$$m = \frac{c - d}{a - b} = \frac{251.9 \cdot 10^{-6} A}{4V} = 6.30 \cdot 10^{-5} S$$

An equation of the line can be found using point-slope form  $y - y_1 = m(x - x_1)$ . The  $X_b, Y_d$  point is selected but any of the two points may be used.

$$I_C - 6.356 \cdot 10^{-3} = 6.30 \cdot 10^{-5} (V_{CE} - 1)$$

Now the early voltage can be found at the x-intercept when  $I_C=0$ :

$$-6.356 \cdot 10^{-3} = 6.30 \cdot 10^{-5} (V_A - 1) \xrightarrow{\text{yields}} V_A = |-100| = 100V$$

$$r_0 = \frac{V_A}{I_C} = \frac{100}{1mA} = \boxed{100k\Omega}$$

#### Comparing Measured value to datasheet values

The measured values of  $\beta$ ,  $r_\pi$ , and  $1/r_0$  all fall in between the minimum and maximum value found in the data sheet for the 2N3904 transistor.

#### c) Biasing

##### Biassing from measured plot (i)


The measured parameters from the curves are  $\beta = 118$  and  $V_{BE} = 0.65V$ .

In addition,  $V_{CC} = 15V$ ,  $I_C = 1mA$ ,  $V_{CE} < 4V$ ,  $R_E = R_C/2$ . The other currents may be determined as follows:

$$I_B = \frac{I_C}{\beta} = \frac{1mA}{118} = 8.47\mu A$$

$$I_E = I_B + I_C = 8.47\mu A + 1mA = 1.0084mA$$

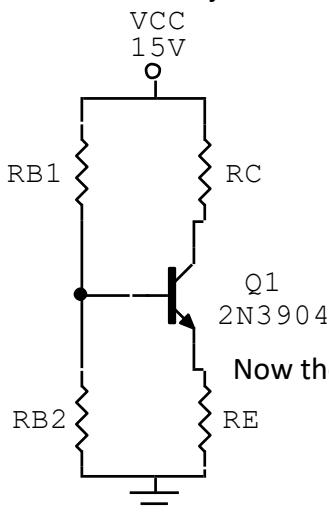Next  $R_C$  and  $R_E$  can be determined by doing KVL from  $V_{CC}$  to ground across the collector-emitter junction.  $V_{CE}$  can be set to 3V since it is less than 4V.



$$V_{CC} = I_C R_C + I_E R_E + V_{CE} = I_C R_C + \frac{1}{2} I_E R_C + V_{CE}$$

$$\xrightarrow{\text{yields}} R_C = \frac{V_{CC} - V_{CE}}{I_C + \frac{1}{2} I_E} = \frac{15 - 3}{1mA + \frac{1}{2} \cdot 1.0084mA} = 7978\Omega$$

$$R_E = \frac{R_C}{2} = 3989\Omega$$

Now the voltage of the emitter, collector, and base can be calculated.

$$V_E = I_E R_E = 1.0084mA \cdot 3989\Omega = 4.022V$$

$$V_C = V_E + V_{CE} = 4.022V + 3V = 7.022V$$

$$V_B = V_E + V_{BE} = 4.012V + 0.65V = 4.662V$$

The following 2 equations can be used to determine the values of  $R_{B1}$  and  $R_{B2}$ .

$$KCL: \frac{V_{CC} - V_B}{R_{B1}} = I_B + \frac{V_B}{R_{B2}}$$

$$KVL: V_{CC} \left( \frac{R_{B2}}{R_{B1} + R_{B2}} \right) - I_B(R_{B1} || R_{B2}) - V_B = 0$$

These equations do not provide a unique solution, so I arbitrarily chose  $R_{B1}=10k\Omega$  which gives

$R_{B2}=4.55 k\Omega$ .

| $R_C$         | $R_E$         | $R_{B1}$     | $R_{B2}$       |
|---------------|---------------|--------------|----------------|
| 7978 $\Omega$ | 3989 $\Omega$ | 10k $\Omega$ | 4.55k $\Omega$ |

Here are the results of the simulation for the d.c operating point for the 2N3904.

| $I_C$         | $I_B$         | $I_E$   | $V_B$  | $V_C$  | $V_E$  |
|---------------|---------------|---------|--------|--------|--------|
| 998.6 $\mu A$ | 8.590 $\mu A$ | 1.007mA | 4.664V | 7.034V | 4.017V |

Biassing using the 1/3 rule (ii)

I will use the first version of the 1/3 rule which states that:

$$V_B = \frac{1}{3}V_{CC} = 5V, V_C = \frac{2}{3}V_{CC} = 10V, I_1 = \frac{I_E}{\sqrt{\beta}}$$

Using  $\beta = 118$  and  $V_{BE} = 0.65V$  we find that  $V_E = V_B - V_{BE} = 4.35V$

Subsequently the currents are calculated

$$I_B = \frac{I_C}{\beta} = \frac{1mA}{118} = 8.47\mu A$$

$$I_E = I_B + I_C = 8.47\mu A + 1mA = 1.0084mA$$

$$I_1 = \frac{I_E}{\sqrt{\beta}} = \frac{1.0084mA}{\sqrt{118}} = 92.83\mu A$$

$$I_2 = I_1 - I_B = 92.83\mu A - 8.47\mu A = 84.36\mu A$$

Finally, the resistances are calculated

$$R_C = \frac{V_{CC} - V_C}{I_C} = 5k\Omega$$

$$R_E = \frac{V_E}{I_E} = \frac{4.35V}{1.0084mA} = 4.314k\Omega$$

$$R_{B1} = \frac{V_{CC} - V_B}{I_1} = \frac{10V}{92.83\mu A} = 107.72k\Omega$$

$$R_{B2} = \frac{V_B}{I_2} = \frac{5V}{84.36\mu A} = 59.27k\Omega$$

The d.c operating point values of the biased circuit using the 1/3 rule is shown below.

| $I_C$   | $I_B$         | $I_E$   | $V_B$  | $V_C$  | $V_E$  |
|---------|---------------|---------|--------|--------|--------|
| 1.001mA | 8.431 $\mu$ A | 1.010mA | 5.002V | 9.994V | 4.356V |

Using standard resistors (iii)

Replace the resistances calculated using the 1/3 rule with standard resistors.

$$R_C = 5.1k\Omega, R_E = 4.3k\Omega, R_{B1} = 110k\Omega, R_{B2} = 62k\Omega$$

| $I_C$   | $I_B$         | $I_E$   | $V_B$  | $V_C$  | $V_E$  |
|---------|---------------|---------|--------|--------|--------|
| 1.020mA | 8.575 $\mu$ A | 1.028mA | 5.067V | 9.801V | 4.420V |

Every method biases the circuit correctly however using the 1/3 rule is much faster and still provides accurate results while allowing versatility when selecting the resistances.

d) 2N2222A and 2N4401 d.c operating points (iv)

Using the same standard resistance values, we replace the 2N3904 with the 2N2222A and 2N4401 and measure their d.c operating points.

|               | $I_C$   | $I_B$         | $I_E$   | $V_B$  | $V_C$  | $V_E$  |
|---------------|---------|---------------|---------|--------|--------|--------|
| <u>2N3904</u> | 1.020mA | 8.575 $\mu$ A | 1.028mA | 5.067V | 9.801V | 4.420V |
| <u>2N222A</u> | 1.055mA | 6.285 $\mu$ A | 1.061mA | 5.158V | 9.629V | 4.556V |
| <u>2N4401</u> | 1.035mA | 6.971 $\mu$ A | 1.042mA | 5.131V | 9.731V | 4.472V |


The BJTs are still biased properly in the active region. Therefore the 1/3 rule is a valid method of biasing BJTs even with different  $\beta$  values.



## Part 2
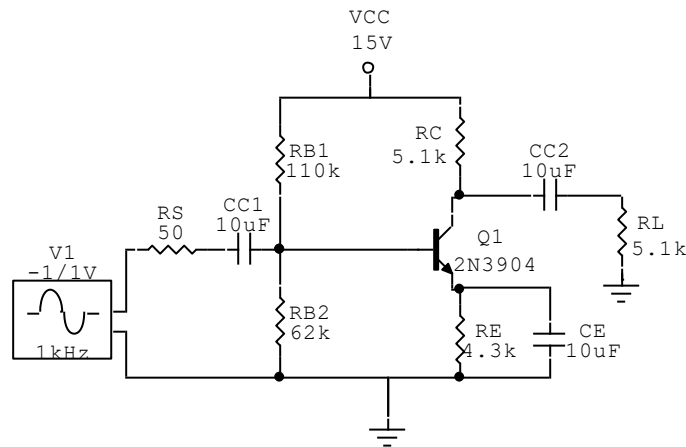
### a) 2N3904 & 2N4401 Common Emitter Amplifier

Here is the biased common emitter amplifier using the **2N3904**.




The magnitude and phase(degrees) bode plots are included in the appendix simulated from 1mHz to 100GHz. Calculate  $C_\pi$  and  $C_\mu$  using the d.c operating point  $g_m=0.04S$  and  $V_{CB} = 5V$  and the SPICE model parameters of the **2N3904**.

$$C_\pi = 2 \cdot C_{JE} + TF \cdot g_m = 2 \cdot 4.5pF + 400ps \cdot 0.04 = 25pF$$


$$C_\mu = \frac{C_{JC}}{\left(1 + \frac{V_B}{V_{JC}}\right)^{M_{JC}}} = \frac{3.5pF}{\left(1 + \frac{5}{0.75}\right)^{0.330}} \approx 2pF$$

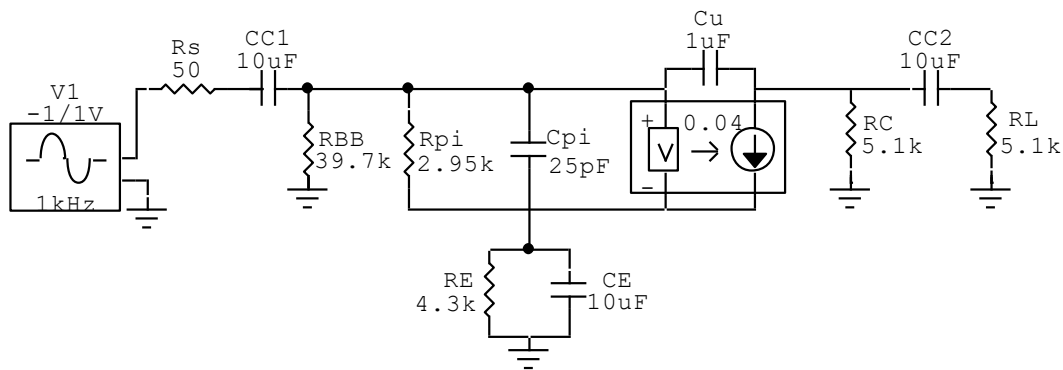The complete small-signal model is created for the **2N3904**. Recall  $r_\pi = 2950\Omega$  and  $\beta=118$  from part 1.



Applying Miller's theorem and Thevenin equivalent for the CE amplifier like in the course notes can yield the zeros and poles. There are two coupling capacitors so it is known that there will be 2 low

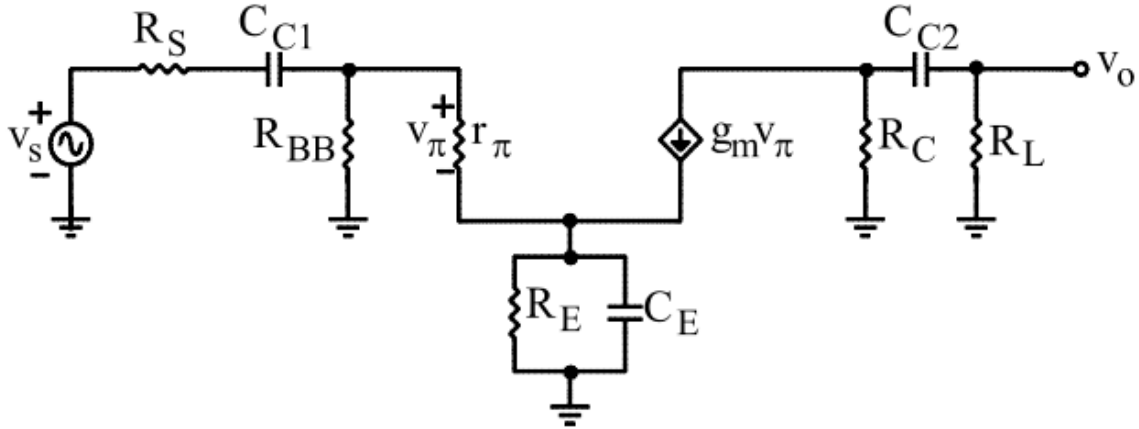frequency zeros at zero. This is the Low Frequency Small-Signal Model.



$$f_{Lz1} = f_{Lz2} = 0 \text{ Hz}$$


$$f_{Lz3} = \frac{1}{2\pi R_E C_E} = 3.70 \text{ Hz}$$

$$f_{Lp2} = \frac{1}{2\pi (R_C + R_L) C_{C2}} = 1.56 \text{ Hz}$$

$$f_{Lp1} = \frac{1}{2\pi (R_S + R_{BB} || (r_\pi + (1 + \beta) R_E)) C_{C1}} = 432 \text{ mHz}$$

$$f_{Lp3} = \frac{1}{2\pi C_E \left( \left( \frac{r_\pi + R_{BB} || R_S}{1 + \beta} \right) || R_E \right)} = 635 \text{ Hz}$$

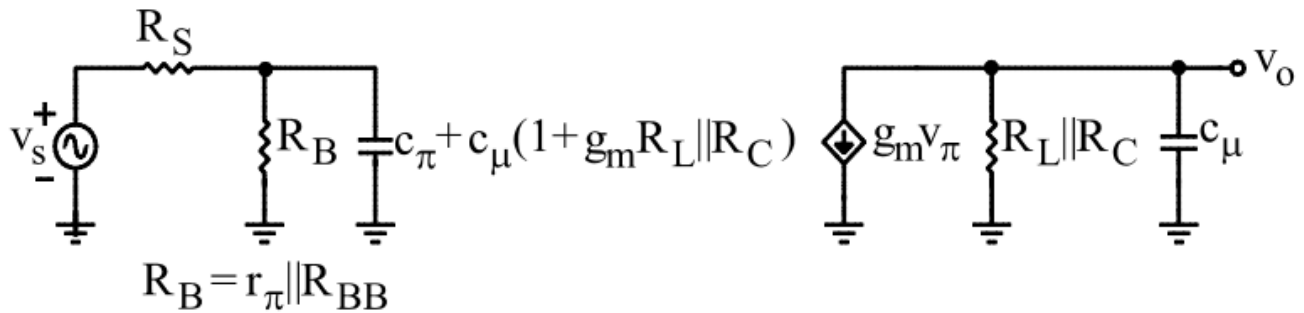
This is the High Frequency Small-Signal Model.



$$f_{Hp1} = \frac{1}{2\pi ((R_{BB} || r_\pi) || R_S) (c_\pi + g_m \cdot R_L || R_C)} = 15.5 \text{ MHz}$$

$$f_{Hp2} = \frac{1}{2\pi (R_C || R_L) c_\mu} = 34.9 \text{ MHz}$$

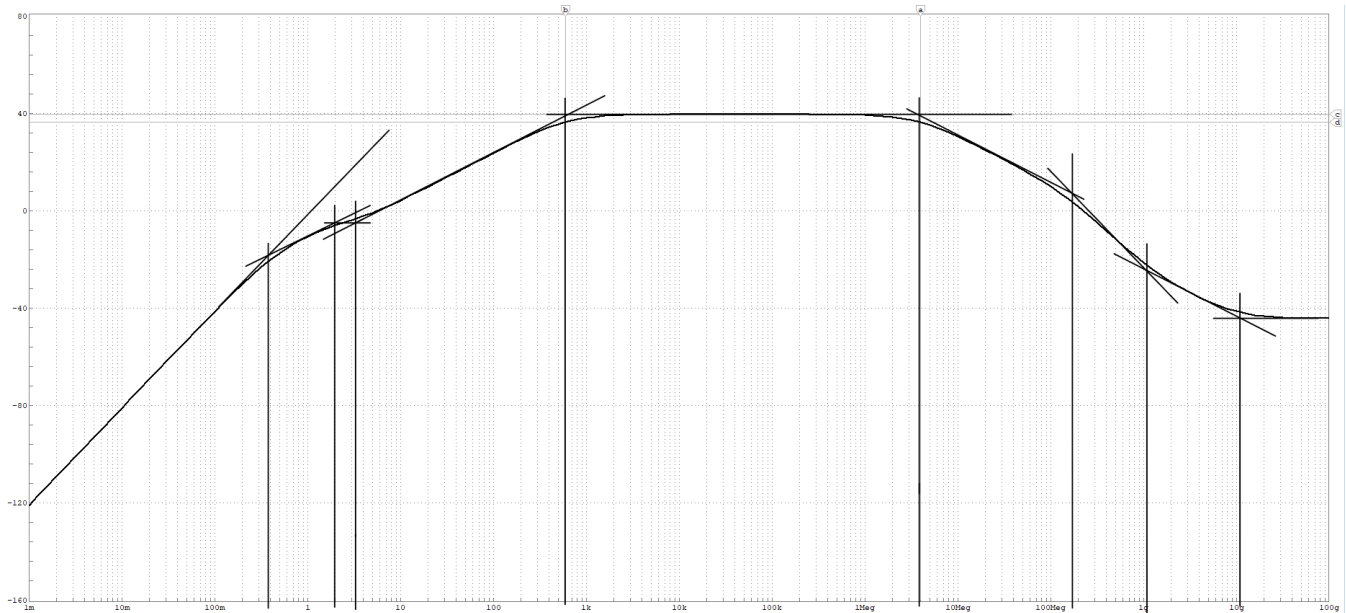Here are the locations of the poles and zeros estimated using linear approximation.




This table summarizes the calculated and graphically measured locations of the poles and zeros in Hz.

| <i>2N3904</i> | $f_{Lz1}$ | $f_{Lz2}$ | $f_{Lp1}$ | $f_{Lp2}$ | $f_{Lz3}$ | $f_{Lp3}$ | $f_{Hp1}$ | $f_{Hp2}$ | $f_{Hz1}$ |
|---------------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|
| Calculated    | 0         | 0         | 0.432     | 1.56      | 3.70      | 635       | 15.5M     | 34.9M     | $\infty$  |
| Measured      | 0         | 0         | 0.400     | 2.2       | 4         | 600       | 10M       | 600M      | 5G        |
| % error       | 0         | 0         | 8%        | 29.1%     | 7.5%      | 5.83%     | 55%       | 94.1%     |           |

The graphically measured values are quite like the calculated values other than the high frequency poles. There was also a high frequency zero in the simulated result.

Now replace the *2N3904* with the *2N4401*. The magnitude and phase bode plots simulated from 1mHz to 100GHz for the *2N4401* are included in the appendix. Recalculate the location of the poles and zeros the same way as done before, except with new parameters for the parasitic capacitances of the *2N4401*, and then recalculate  $\beta$  and  $r_{\pi}$ .  $\beta = 148$ ,  $r_{\pi} = 3586\Omega$ .  $C_{\pi}=67.28\text{pF}$ ,  $C_{\mu}=5.2\text{pF}$ .

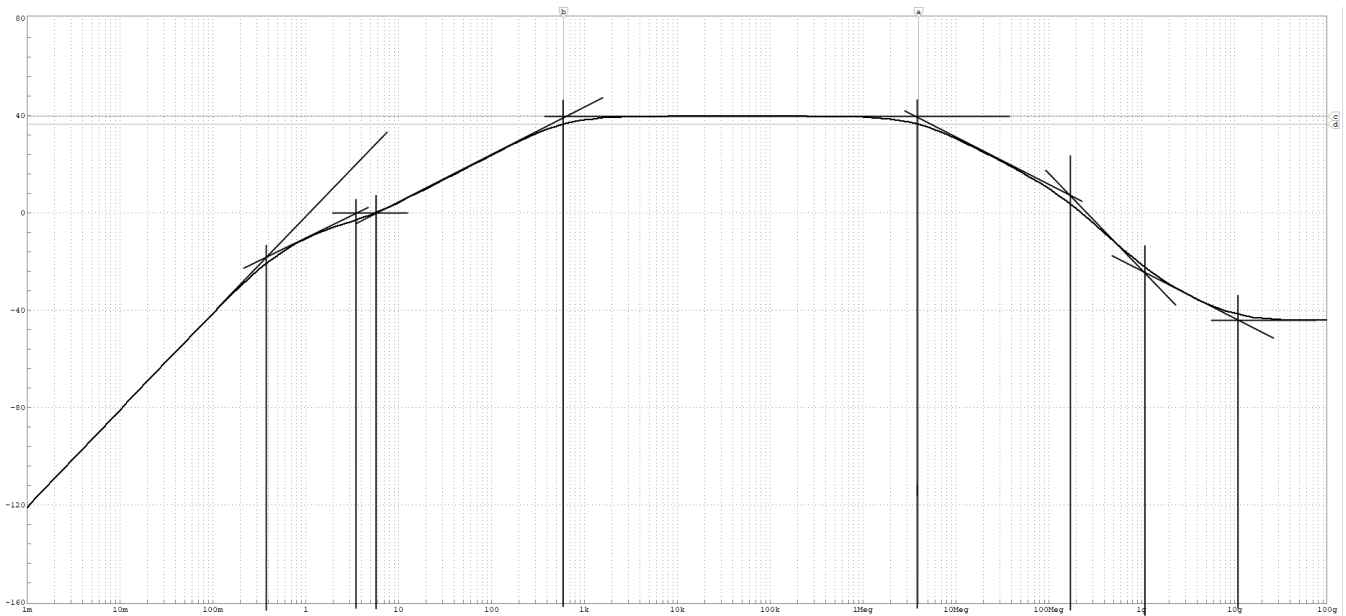Then, graphically measure the poles/zeros with linear approximation and compare with the calculated.




Here are the calculated and graphically measured frequencies in Hz for the 2N4401.


| 2N4401     | $f_{Lz1}$ | $f_{Lz2}$ | $f_{Lp1}$ | $f_{Lp2}$ | $f_{Lz3}$ | $f_{Lp3}$ | $f_{Hp1}$ | $f_{Hp2}$ | $f_{Hz1}$ | $f_{Hz2}$ |
|------------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|
| Calculated | 0         | 0         | 0.426     | 1.56      | 3.70      | 655       | 5.19M     | 11.9M     | $\infty$  | $\infty$  |
| Measured   | 0         | 0         | 0.390     | 2         | 3.40      | 600       | 4M        | 190M      | 1G        | 10G       |
| % error    | 0         | 0         | 9.23%     | 22%       | 8.82%     | 9.17%     | 29.8%     | 93.7%     |           |           |

Again, the graphically measured values are quite like the calculated values other than the high frequency poles. There are also two a high frequency zero in the simulated result.
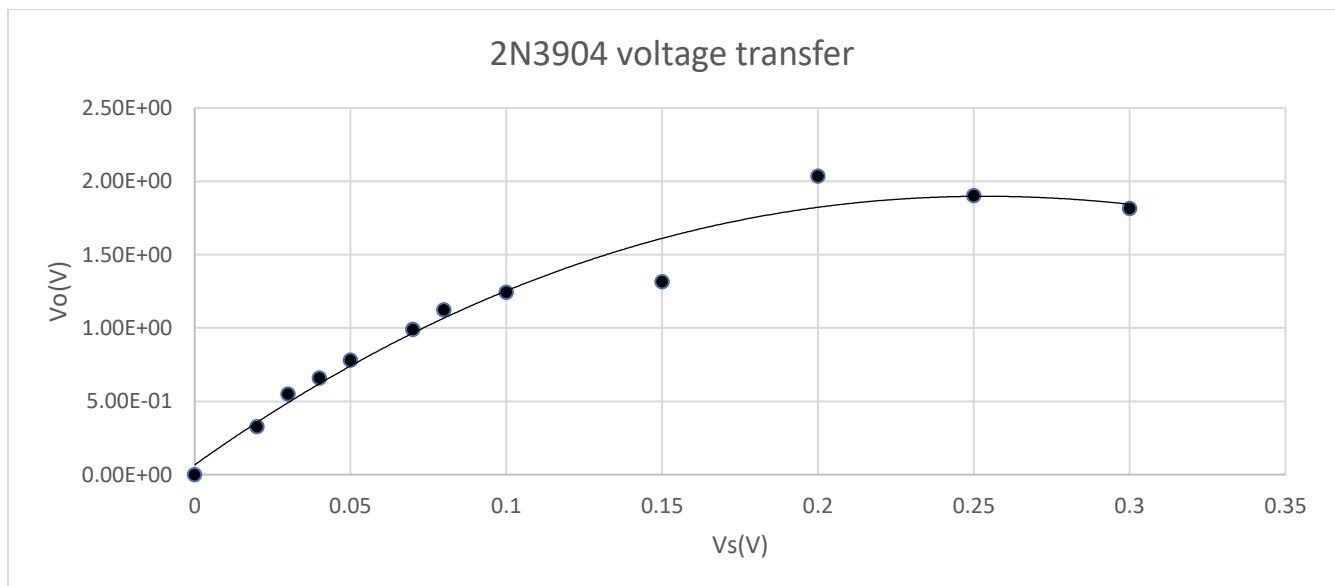
#### b) Midband Voltage Transfer Curve

A midband frequency of 100kHz is selected for this test. The input voltage source amplitude is varied from 0-0.3V.




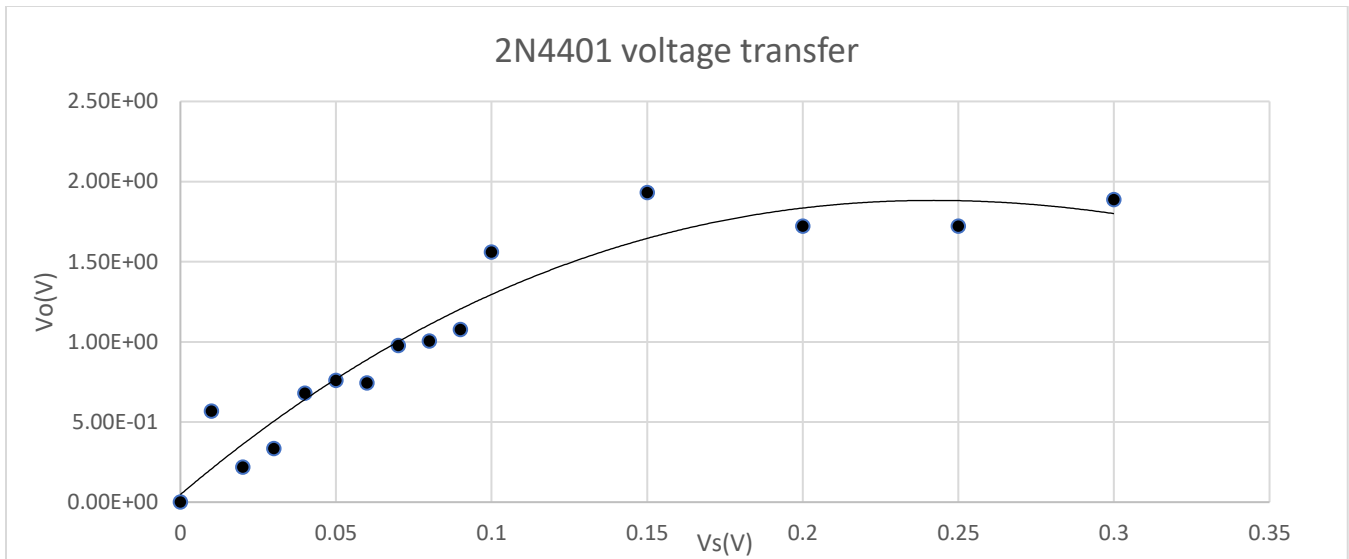

The non-linear behavior starts to happen around 0.1V for both transistors.

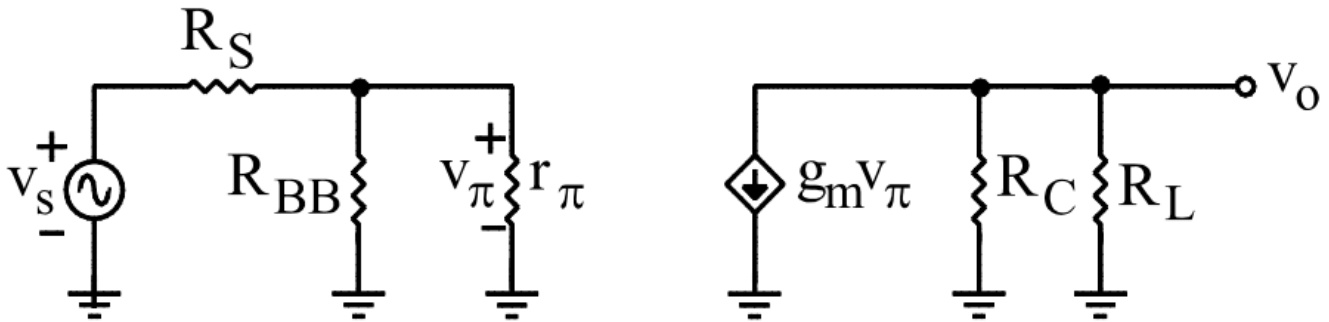c) Midband Input Impedance

Here is the circuit at midband.  $C_E$  will be shorted, and so the emitter will be grounded.



The input impedance for the *2N3904* can be calculated as  $Z_{in} = R_{BB} || r_{\pi} = \boxed{2745\Omega}$

The input impedance for the *2N4401* is  $Z_{in} = R_{BB} || r_{\pi} = \boxed{3289\Omega}$

To measure the input impedance set the AC source to 100kHz with 1V amplitude and then use the AC multimeter to measure the input current and base voltage.

$$Z_{in} = \frac{V_B}{I_{in}} = \frac{6.12mV}{1.755\mu A} = \boxed{3487\Omega} \text{ (2N3904)}$$

$$Z_{in} = \frac{V_B}{I_{in}} = \frac{6.14mV}{1.379\mu A} = \boxed{4453\Omega} \text{ (2N4401)}$$

d) Midband Output Impedance

At the midband the impedance seen at the output impedance is simply  $R_C$ . A 10mV, 10kHz source is used.

$$Z_{out} = R_C = \boxed{5.1k\Omega}$$

The output impedance is measured by

$$Z_{out} = \frac{V_o}{I_{out}} = \frac{570.1mV}{111.8\mu A} = \boxed{5.1k\Omega} \text{ (2N3904)}$$


$$Z_{out} = \frac{V_o}{I_{out}} = \frac{592.4mV}{116.2\mu A} = \boxed{5.1k\Omega} \text{ (2N4401)}$$

e) Transistor selection

The 2N3904 has a larger bandwidth than the 2N4401 with other characteristics remaining similar. For an amplifier a wider bandwidth gives the best performance, so the 2N3904 should be selected.

### Part 3

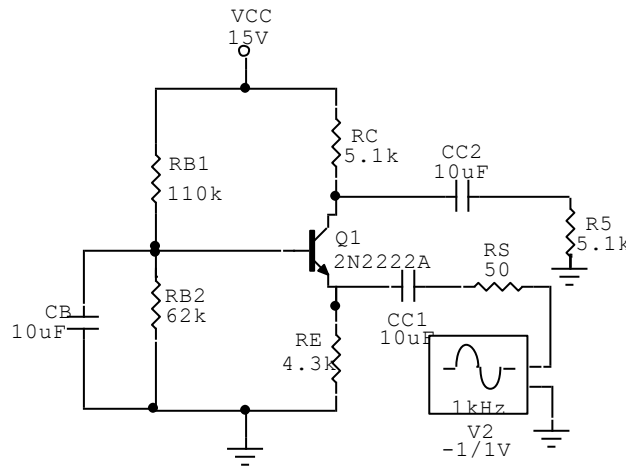a) 2N2222A Common Base Amplifier poles & zeros



Calculate  $c_{\pi}=75.7pF$  and  $c_{\mu}=7.76pF$  with the new circuit parameters. The d.c operating point calculated in part 1 for the 2N2222A can be used to calculate  $\beta = 168$ ,  $g_m = 0.0422$ , and  $r_{\pi} = 3981\Omega$ . There are 2 zeros at zero due to the coupling capacitors. We find the locations of the remaining poles/zeros using formulas taught in the class.

$$f_{Lz1} = f_{Lz2} = 0 \text{ Hz}$$

$$f_{Lz3} = \frac{1}{2\pi R_{BB} C_B} = 0.401 \text{ Hz}$$


$$f_{Lp1} = \frac{1}{2\pi (R_{BB} || (r_{\pi} + (1 + \beta) R_E)) C_B} = 0.423 \text{ Hz}$$


$$f_{Lp2} = \frac{1}{2\pi (R_C + R_L) C_{C2}} = 1.56 \text{ Hz}$$

$$f_{Lp3} = \frac{1}{2\pi \left( \frac{r_\pi}{1+\beta} || R_E + R_S \right) C_{C1}} = 217 \text{ Hz}$$


$$f_{Hp1} = \frac{1}{2\pi (R_C || R_L) c_\mu} = 8.04 \text{ MHz}$$

$$f_{Hp2} = \frac{1}{2\pi \left( \frac{r_\pi}{1+\beta} || R_E || R_S \right) c_\pi} = 132 \text{ MHz}$$

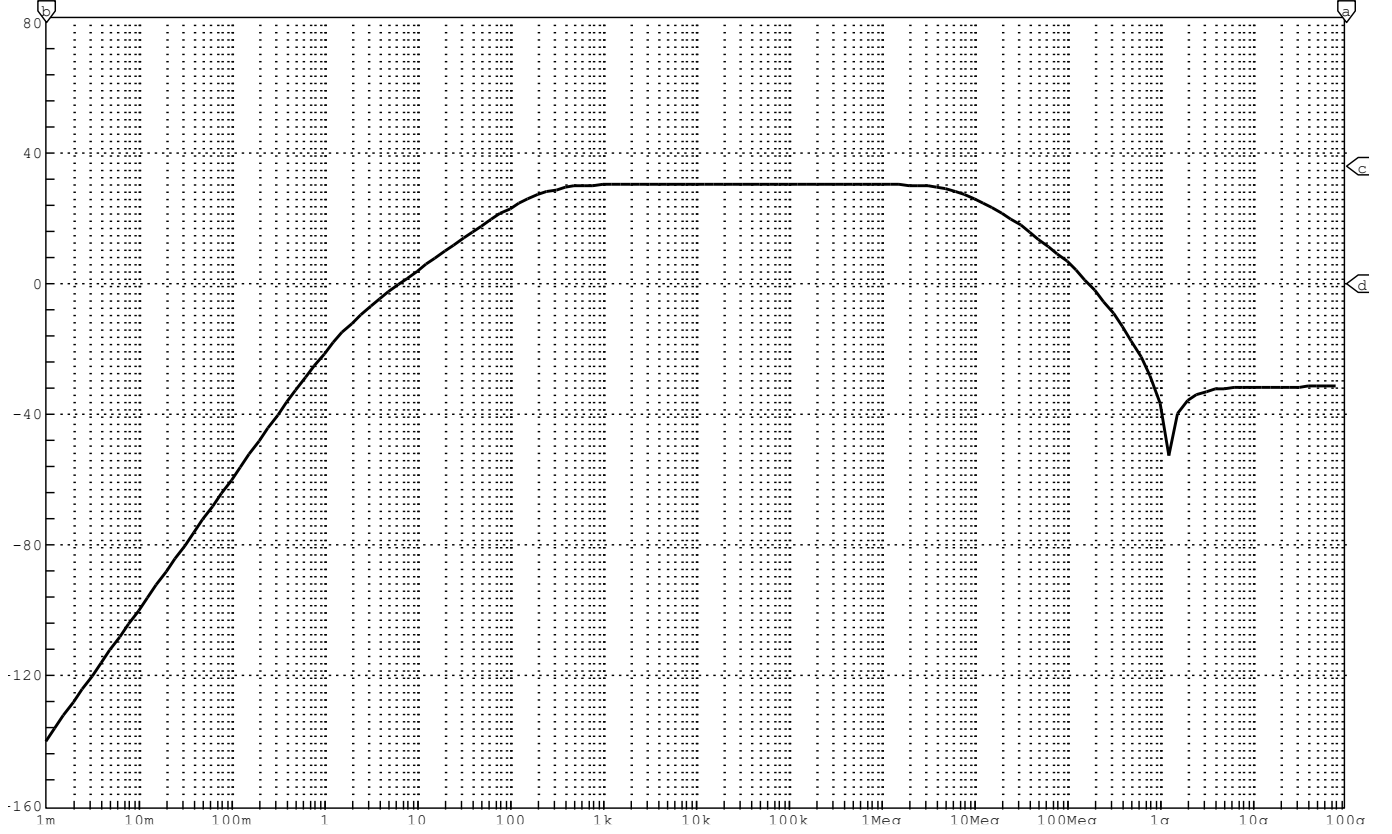

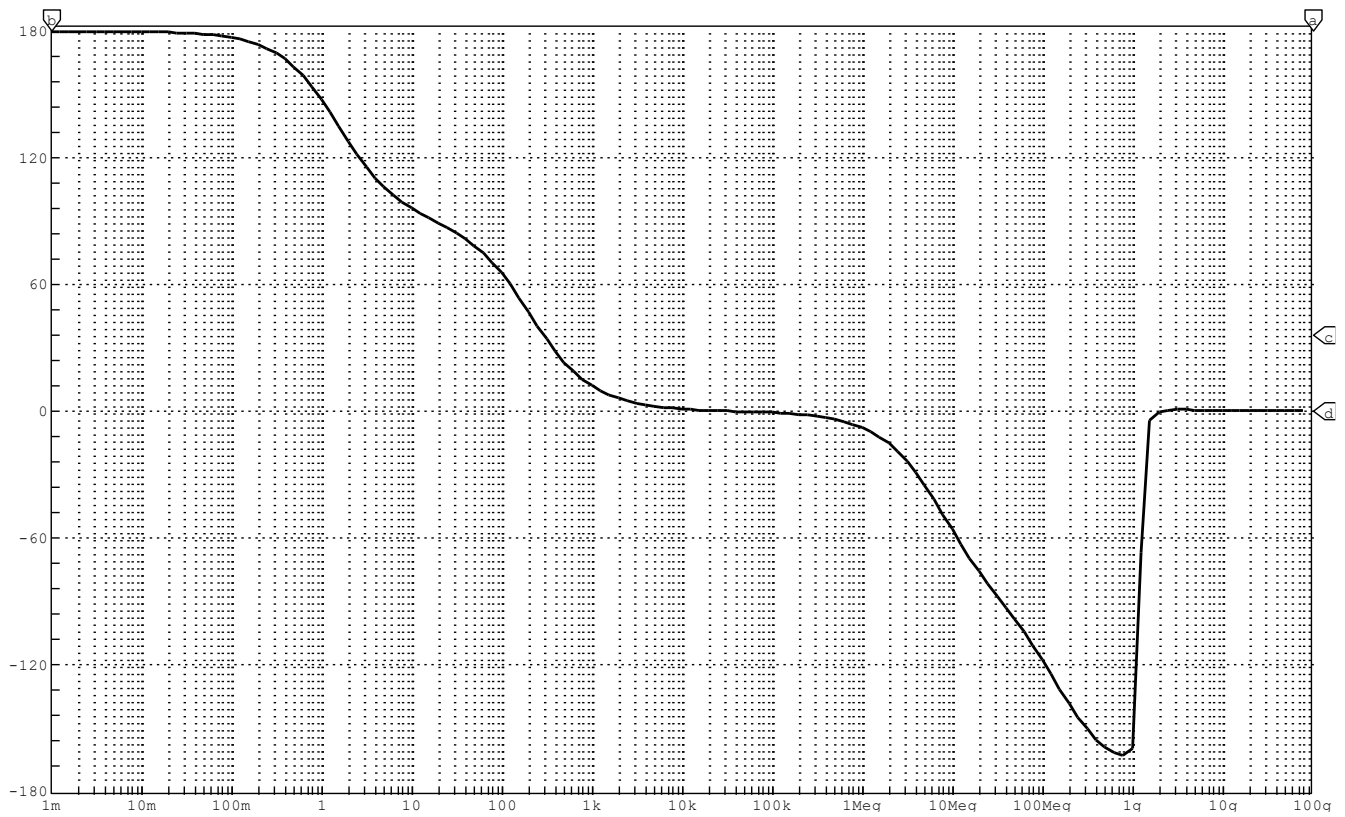

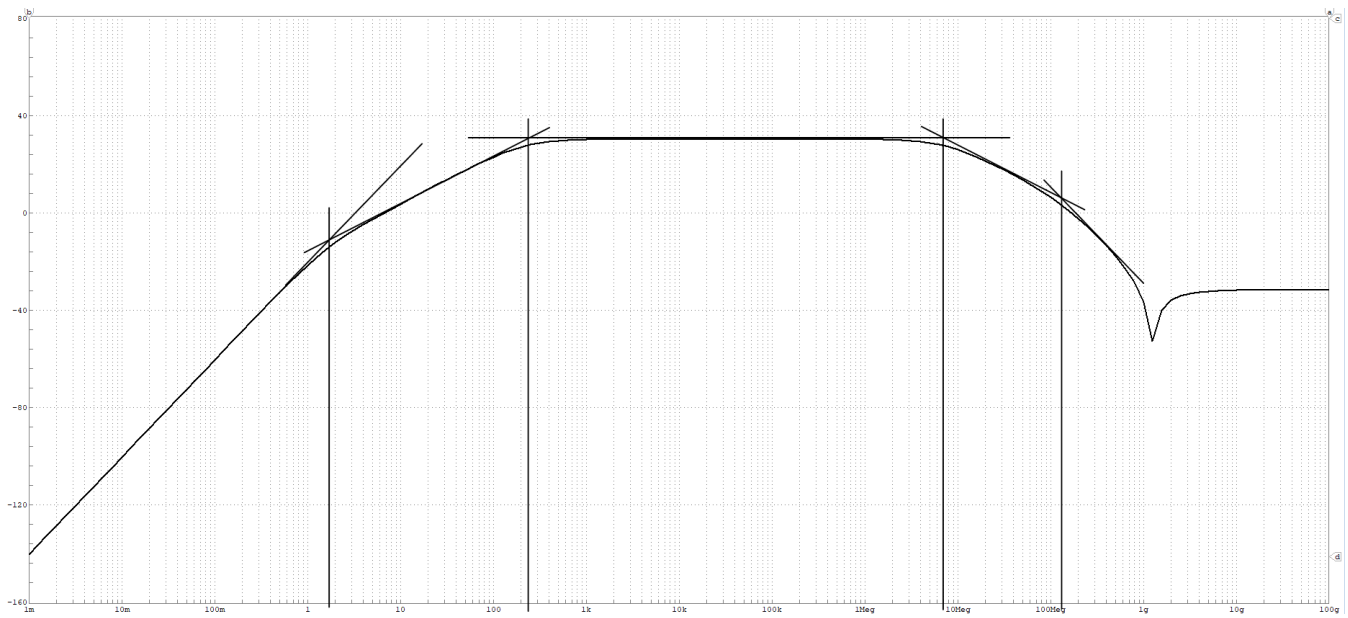Approximate the locations using linear approximation. There must be a low frequency pole and zero that occur in the same location (as shown in the calculations), these are marked in the table by \*.






Here are the calculated and approximated values for the locations of the poles in Hz. The cusp at ~1GHz may be caused by multiple zeros or a complex pole.

| 2N2222A    | $f_{Lz1}$ | $f_{Lz2}$ | $f_{Lz3}$ | $f_{Lp1}$ | $f_{Lp2}$ | $f_{Lp3}$ | $f_{Hp1}$ | $f_{Hp2}$ |
|------------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|
| Calculated | 0         | 0         | 0.401     | 0.423     | 1.56      | 217       | 8.04M     | 132M      |
| Measured   | 0         | 0         | 0.401*    | 0.423*    | 1.80      | 220       | 8M        | 130M      |
| % error    | 0         | 0         | 0         | 0         | 13.3%     | 1.36%     | 0.5%      | 1.54%     |
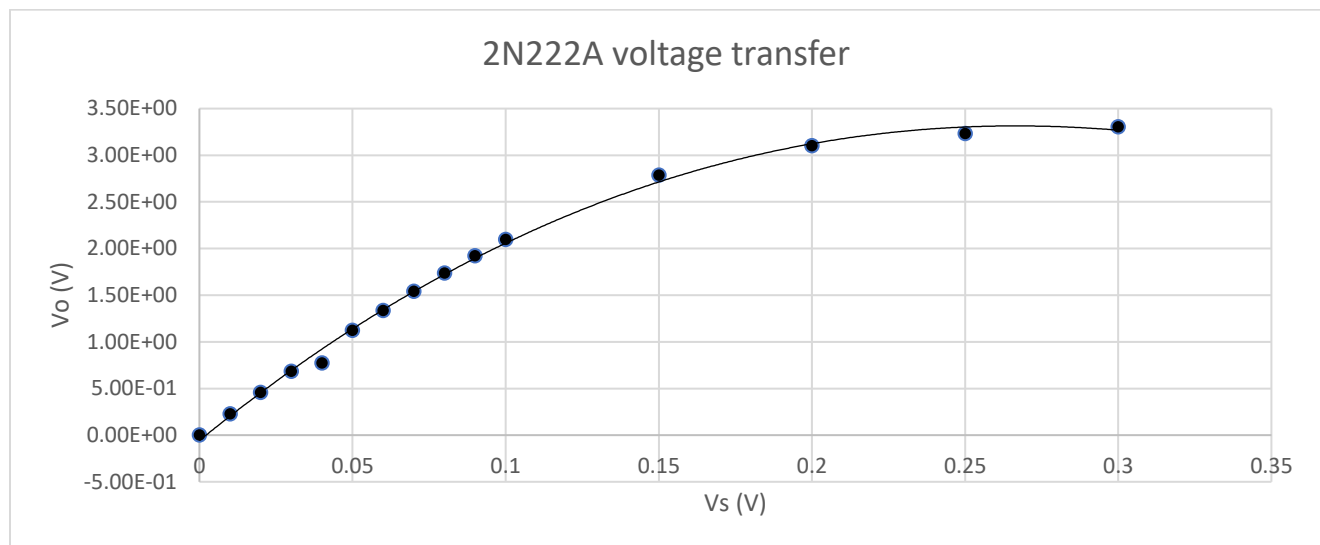
#### b) Voltage Transfer Curve

Use a 1kHz source and vary the amplitude. It starts to become non-linear at around  $V_s = 0.1V$ .



#### c) Midband Input Impedance

Calculate the input impedance as  $Z_{in} = R_E || \frac{1}{1+\beta} r_{\pi} = \boxed{23.4\Omega}$

To measure the input impedance, short the source resistance and apply a source with 10mV amplitude and 100kHz frequency. Use the AC RMS multimeter to measure the emitter voltage and input current.

$$Z_{in} = \frac{V_E}{I_{in}} = \frac{1.011mV}{40.09\mu A} = \boxed{25.2\Omega}$$

#### d) Midband Output Impedance

The output impedance is simply  $Z_{out} = R_C = \boxed{5.1k\Omega}$

$$Z_{out} = \frac{V_C}{I_{in}} = \frac{70.36mV}{13.97\mu A} = \boxed{5.04k\Omega}$$


## References

1. ELEC 301 Course Notes
2. A. Sedra and K. Smith, "Microelectronic Circuits," 5 th (or higher) Ed., Oxford University Press, New York
3. CircuitMaker™ User's Manual
4. 2N3904 datasheet [<https://datasheetspdf.com/pdf-file/1114626/Motorola/2N3904/1>]
5. Standard Resistor and Capacitor Values

## Appendix

### Part 2a:

2N3904 magnitude/phase bode plot:

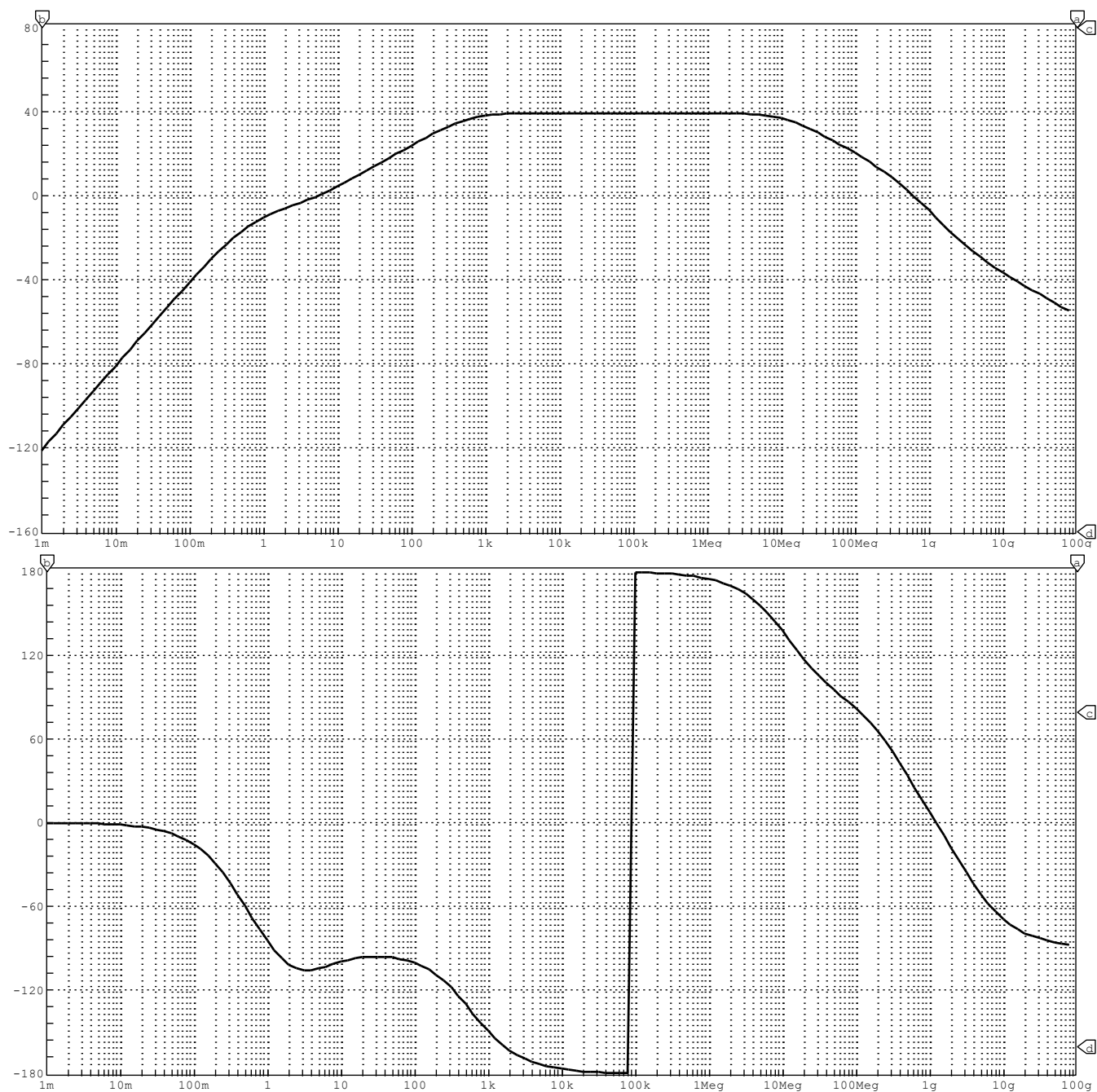

2N4401 magnitude/phase bode plot:

